

# EXAM #2

---

---


---

---

---



# LECTURE (09/28/2023)

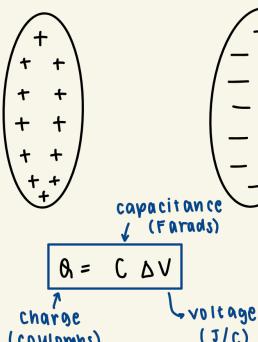


$$C = K \frac{\epsilon_0 A}{d}$$

$$Q \propto \Delta V$$

charge

C does NOT depend on  $\Delta V$  or charge

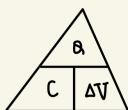
BUT depends on geometry of capacitor A, d & dielectric K



By changing two plates + & - we now have  $\Delta V$  (<sup>Potential difference</sup>)

## Calculating capacities

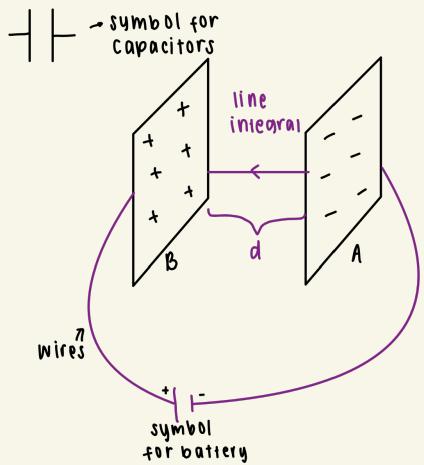- #1) Assume the capacitor has a charge  $Q$ ,
- #2) determine the  $\vec{E}$  field (Electric field) between the conductors (You can use Gauss's Law for symmetry)
- #3) Find the potential difference between the conductors.
- #4) Then use  $C = \frac{Q}{\Delta V}$



#1)  $Q$  ON CAPACITOR

#2)  $E = \frac{Q}{\epsilon_0 A} = \frac{Q/A}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$

#3)  $\Delta V = - \int_A^B \vec{E} \cdot d\vec{l}$

$V_B - V_A = - E L \Big|_A^B$

$= - E (B-A)$

$$\Delta V = Ed$$

$$\Delta V = \frac{Q}{A \epsilon_0} d$$

#4.


$C = \frac{Q}{\Delta V}$
$C = \frac{\epsilon_0 A}{d}$

## Connection between $\vec{E}$ & $V$

$$\Delta V = Ed$$

$$\vec{E} = -\frac{\partial V}{\partial r}$$
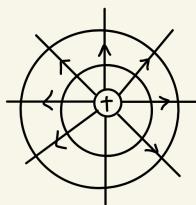
$$\vec{E} = \left\langle -\frac{\partial V}{\partial x}, -\frac{\partial V}{\partial y}, -\frac{\partial V}{\partial z} \right\rangle$$




→ direction of decreasing potential

If field is only in  $E_x$ , then:

$$E_x = -\frac{\Delta V}{\Delta x} \rightarrow \text{The } (-) \text{ gradient of the potential is the electric field}$$

# LECTURE (10/10/2023)

## Capacitors

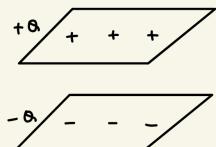

$$\equiv \begin{array}{c} + \\ | \\ - \end{array}$$

Capacitance does **NOT** depend on charge & voltage

$\Rightarrow$  what does capacitance depend on?

Area, Distance( $d$ ) in between & Dielectric constant  $K$

$$C = K \epsilon_0 \frac{A}{d}$$

distance between plates

$$C = \frac{Q}{\Delta V} \quad \Leftrightarrow \quad Q = C \Delta V$$

## Energy stored in a capacitor

$$U_{\text{capacitor}} = \frac{1}{2} Q_i \Delta V$$

(Joules)


$C$

$Q_i$

$e^-$  is moving downwards

... when we started our conversation about potential (Electric)

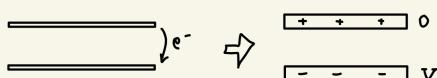
$$V = \frac{U}{Q} \quad \Leftrightarrow \quad U = QV$$



$$\text{Average voltage} \times Q_i = \text{Total Energy}$$

$$\frac{1}{2} \Delta V \times Q_i = \text{Energy or } U$$

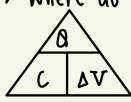$\Rightarrow$  Where do we get this equation from?



$$U = \frac{Q_i}{C}$$

$$U = \int_0^Q dU = \int_0^Q V dq$$

$$U = \int_0^Q V dq = \int_0^Q \frac{q}{C} dq = \frac{1}{C} \int_0^Q q dq = \frac{Q^2}{2C}$$

$$U = \frac{1}{2} \frac{Q^2}{C} \rightarrow \text{has only } Q \& \Delta V = \frac{1}{2} Q_i \Delta V$$

$$\rightarrow \text{has } C, \Delta V = \frac{1}{2} \Delta V (C \cdot \Delta V) = \frac{1}{2} C \Delta V^2$$

$$\text{Energy} \Rightarrow \frac{U}{\text{vol}} = U$$

energy density =  $\frac{1}{2} \epsilon_0 E^2$

$$U = \frac{1}{2} C \Delta V^2$$

$$E = -\frac{\Delta V}{\Delta x}$$


$$\text{Energy density} = \frac{1}{2} \cdot \frac{\epsilon_0 A}{d} (Ed)^2$$

$$= \frac{1}{2} \epsilon_0 E^2 (A \cdot d)$$

volume (v)


$$U = \frac{U}{\text{vol}} = \frac{1}{2} \epsilon_0 E^2 v$$

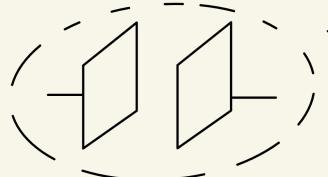\* if capacitor is not connected to battery = isolated



→ not connected = isolated

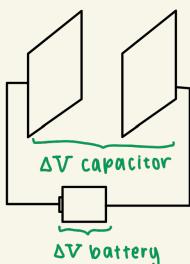
→ if you charge it & disconnect, we assume charges will still be the same.



→ connected - NOT isolated

$$\Delta V_{\text{capacitor}} = \Delta V_{\text{battery}}$$

→ charges are always the same

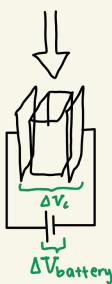


$$\Delta V_{\text{battery}} = \Delta V_{\text{capacitor}}$$

⇒ what happens to E? decreases/increases/stays the same

Why a dielectric?


- isolate the 2 plates (insulator)

- capacitance increases  $C \uparrow$

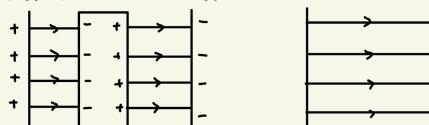


• E will stay the same as  $V = E \cdot d$  or  $\Phi = C \Delta V$ . Additionally, it is hooked up to the battery.

Without the battery, E will decrease.

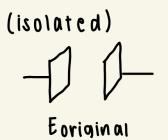


$$\frac{E_{\text{original}}}{E_{\text{dielectric}}} = K$$

(not isolated)

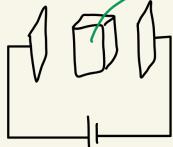

$E_{\text{dielectric}}$  stays the same  
(more charge dumped on the plates)

## LECTURE (10/12/2023)

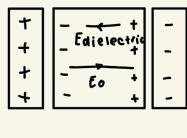


$E_{\text{dielectric}} < E_{\text{original}}$

$$\frac{E_{\text{original}}}{E_{\text{dielectric}}} = K \quad \text{dielectric constant}$$

Adding Capacitors: Series & Parallel Capacitors

$$Q_i = C_i \Delta V$$

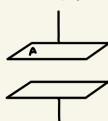


$$\rightarrow \text{Remember! } \frac{Q_i}{C_i \Delta V}$$

$$C = \frac{K \epsilon_0 A}{d}$$

$$C_{\text{series}} \Rightarrow \frac{1}{C_{\text{tot}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

$$C_{\text{parallel}} \Rightarrow C_{\text{tot}} = C_1 + C_2 + \dots + C_n$$

Circuits in Series

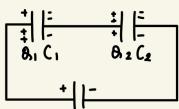

Principle  $\rightarrow Q_1 = Q_2$   
current flow of charge  $\rightarrow I_1 = I_2$

$$\Delta V_{\text{total}} = \Delta V_1 + \Delta V_2$$


$$\frac{Q_{\text{total}}}{C_{\text{total}}} = \frac{Q_1}{C_1} + \frac{Q_2}{C_2}$$

$Q_{\text{total}} = Q_1 = Q_2 \rightarrow$  charges in series are the same

$$\frac{Q_{\text{total}}}{C_{\text{total}}} = \frac{Q_{\text{total}}}{C_1} + \frac{Q_{\text{total}}}{C_2}$$

$$\frac{1}{C_{\text{total}}} = \frac{1}{C_1} + \frac{1}{C_2}$$

## Circuits in parallel

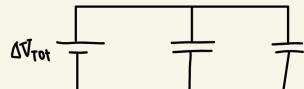

$$\Delta V_{\text{total}} = \Delta V_1 = \Delta V_2$$

$$\Theta_{\text{total}} = \Theta_1 + \Theta_2$$

$$C_{\text{total}} \cdot \Delta V_{\text{total}} = C_1 \Delta V_1 + C_2 \Delta V_2$$

$$C_{\text{total}} \cdot \Delta V_{\text{total}} = C_1 \Delta V_{\text{total}} + C_2 \Delta V_{\text{total}}$$

$$C_{\text{total}} = C_1 + C_2$$


$$\rightarrow C_{\text{eq}} = C_{\text{equivalent}}$$

## RULE

1. Add capacitances & get  $C_{\text{total}} / C_{\text{eq}}$

2. use  $\Theta = C \Delta V$


## LECTURE (10/17/2023)

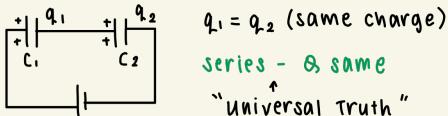

$$q_1 = q_2 \text{ (same charge)}$$

series -  $\Theta$  same

"Universal Truth"

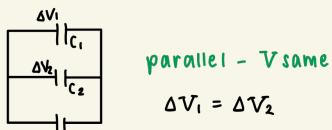


parallel -  $V$  same

$$\Delta V_1 = \Delta V_2$$

## LECTURE (10/19/2023)

► Microscopic look

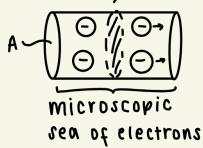


$$I = \frac{\Delta \Theta}{\Delta t} = \frac{C}{S} = \text{Ampere}$$

$$J = \frac{I}{A} \quad \text{Ampere}$$

DYNAMIC → Electrons are moving → needs an electric field

$$\vec{E} \Rightarrow F = q \vec{E}$$

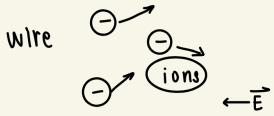

Momentum principle

$$\Delta p = \vec{F}_{\text{net}} \Delta t$$

or  $\vec{F}_{\text{net}} = m \vec{a}$


→ sea of electrons are like swarm of bees. individual bees bounce back & forth, but as a unit they move together.

⇒ Repulsion : Electron-Electron

Attraction : positive ion

⇒ collide w/ atoms

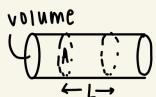⇒ sea of electron speed  $\approx 1 \times 10^{-4} \text{ m/s}$   
(drift speed velocity)



$$I = \frac{\Delta Q}{\Delta t} \rightarrow \text{no. of charges in a certain volume}$$

$$I = \frac{\Delta Q}{\text{volume}} \cdot \frac{\text{volume}}{\Delta t}$$

$$I = \left( \frac{\text{no. of charges}}{\text{volume}} \right) (q_e) \cdot A \cdot \frac{L}{\Delta t}$$

$$I = n \cdot q_e \cdot A \cdot v_{\text{drift}}$$

$\rightarrow n_e$  for electrons

$$\rightarrow \mu E = v_{\text{drift}}$$

Electric field

Examples:

- 1)  $2.30 \times 10^{-18}$  mol of Na (sodium) pass through a cell membrane in  $4.0 \times 10^{-2}$  seconds. Avogadro's number is  $6.02 \times 10^{23}$  ions/mol. Find the current.

$$I = \frac{\Delta Q}{\Delta t} \rightarrow \text{Nions} \cdot q_e$$

$$\text{Nions} = \frac{6.02 \times 10^{23} \text{ ions}}{\text{mol}} \cdot 2.30 \times 10^{-18} \text{ mol} = 13.8 \times 10^5 \text{ ions}$$

$$I = \frac{13.8 \times 10^5 (1.6 \times 10^{-19} \text{ C})}{4.0 \times 10^{-2} \text{ s}} = 5.54 \times 10^{-12} \text{ C/s} \approx 5.54 \text{ pA}$$

- 2) A 5.0 Ampere current flows in a copper wire with cross-sectional area  $1.0 \text{ mm}^2$  carried by electrons with a number density  $n_e = 1.1 \times 10^{29}$  (electrons/ $\text{m}^3$ ). Find the drift speed

$$I = \frac{\Delta Q}{\Delta t}$$

$$I = n_e q_e A v_d$$


$$v_d = \frac{I}{n_e q_e A} = \frac{5 \text{ C/s}}{(1.1 \times 10^{29} \text{ electrons/m}^3) (1.6 \times 10^{-19} \text{ C})(10^{-6} \text{ m}^2)}$$

$$v_d = 2.84 \times 10^{-4} \text{ m/s}$$

Why do we use copper wires instead of any others?

Because in copper, there are a lot of free electrons when compared to other wires, like ions. This will help to make the sea of electrons.

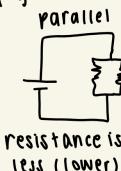If you add resistors in series, it will be bigger. In parallel  $\rightarrow$  less resistance



$$\frac{\Delta V}{I/R}$$

$$\begin{aligned}\Delta V_{\text{total}} &= |\Delta V_1 + \Delta V_2| \\ &= I_1 R_1 + I_2 R_2 \\ I_1 &= I_2 \quad \text{series - } \alpha \text{ (same current)}\end{aligned}$$

$$\frac{\Delta V_{\text{total}}}{I} = \frac{IR_1 + IR_2}{I}$$

$$R_{\text{total}} = R_1 + R_2 \rightarrow \text{series}$$

For parallel...

$$I_{\text{bat}} = I_1 + I_2$$

$$\frac{\Delta V_{\text{total}}}{R_{\text{total}}} = \frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2}$$

$$\Delta V_{\text{total}} = \Delta V_1 = \Delta V_2$$


$$\frac{\Delta V}{R_{\text{tot}}} = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2}$$

$$\frac{1}{R_{\text{tot}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{\text{tot}} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} \longrightarrow \text{parallel}$$

## LECTURE (10/24/2023)

### Chapter 23 Electric Current

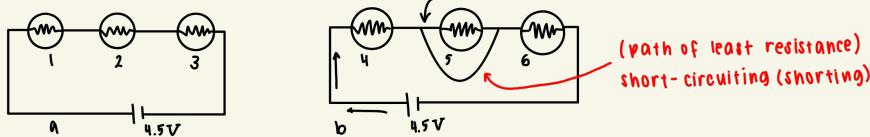


a) In which circuit is the current greater? B

- circuit B because of less resistance


b) A

c) 4+6

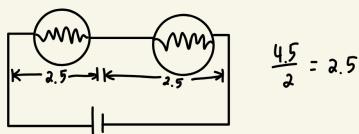
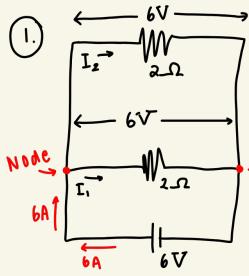
## Principles

- voltages of resistors in parallel are the same.
- current in series are the same



$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_{\text{total}} = \frac{R_1 R_2}{R_1 + R_2} = \frac{2 \times 2}{2+2} = 1 \Omega$$

- currents into the node is equal to the node coming out.

## Kirchhoff's Rule

1. At the node:  $\sum I_{\text{in}} = \sum I_{\text{out}}$  (conservation of charge)

2.  $\sum \Delta V_{\text{loop}} = 0$

- using Kirchhoff's Rules

1) draw circuit diagram

2) assign the direction of the current



↳ If you know the direction, use it

↳ If you don't, assign one (make an arbitrary choice)

↳ If it ends (-) then you chose the "wrong direction"

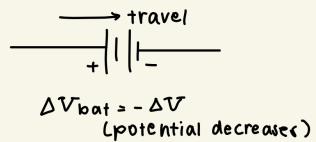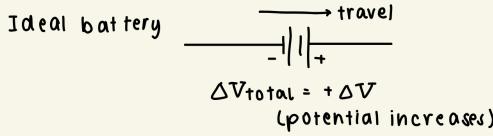3) Travel around the loop

↳ start at one point & go all the way + back to that point.



- For resistor


a)

potential decreases

$$\Delta V_R = -IR$$

$$\Delta V_R = +IR$$

Q.2

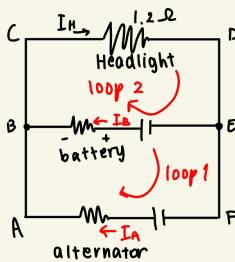

$$\sum I_{in} = \sum I_{out} \quad \text{Equation 1}$$

choose B (node)

$$I_{in} = I_A + I_B = \frac{I_H}{R_H} \quad \text{Equation 1}$$

EBCDE

$$\Delta V_{12} - \Delta V_{0.01,2} - \Delta V_{1,2,2} = 0$$

$$12V - I_B(0.01) - I_H(1.2) = 0 \quad \text{Equation 2}$$

$$\begin{aligned} &FABEF \\ &+ \Delta V_{14} - \Delta V_{0.1,2} + \Delta V_{0.01} - \Delta V_{12} = 0 \end{aligned}$$

$$14V - I_A(0.1) + I_B(0.01) - 12V = 0 \quad \text{Equation 3}$$

$$I_A + I_B - I_H = 0$$

$$0I_A - 0.01I_B - 1.2I_H = -12V$$

$$-0.1I_A + 0.01I_B + 0I_H = -2V$$

$$\begin{pmatrix} 1 & 1 & -1 & 0 \\ 0 & -0.01 & -1.2 & -12 \\ -0.1 & 0.01 & 0 & -2 \end{pmatrix}$$

$$\begin{pmatrix} 1 & 1 & -1 \\ 0 & -0.01 & -1.2 \\ -0.1 & 0.01 & 0 \end{pmatrix} \begin{pmatrix} I_A \\ I_B \\ I_H \end{pmatrix} = \begin{pmatrix} 0 \\ -12 \\ -2 \end{pmatrix}$$

Matrix calc.org

## LECTURE (10/26/2023)

### RC circuits

$$\text{charging} \rightarrow q(t) = q_{\max} (1 - e^{-t/RC})$$

$$\text{discharging} \rightarrow q(t) = q_{\max} e^{-t/RC}$$

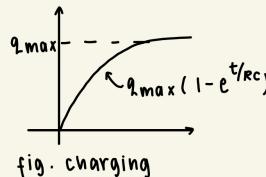


fig. charging



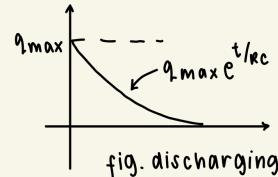
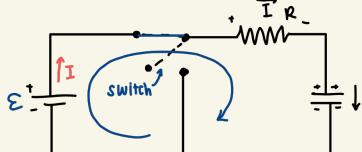


fig. discharging

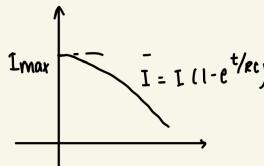
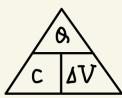
$$\text{Kirchhoff's Rule: } +\varepsilon + IR - \Delta V_C = 0 \quad (\Sigma V = 0)$$



$$+E - IR - \frac{q}{C}$$

current is changing because there is capacitor

$$\frac{+E}{R} - \frac{dq}{dt} \frac{R}{R} - \frac{q}{C} \frac{R}{R} = 0$$

$$\frac{E}{R} - \frac{dq}{dt} - \frac{q}{RC} = 0$$

$$\frac{dq}{dt} = \frac{E}{R} - \frac{q}{RC}$$

$$\frac{dq}{dt} = \frac{EC - q}{RC}$$

$$dq = (EC - q) \frac{dt}{RC}$$

$$\frac{dt}{RC} = \frac{dq}{EC - q}$$

$$\int_0^t \frac{dt}{RC} = \int_0^q \frac{dq}{EC - q} \quad \text{let } u = EC - q \\ du = -dq$$

$$= \int_0^q \frac{1}{u} - du$$

$$= - \ln |EC - q| \Big|_0^q$$

$$= -(\ln |EC - q| - \ln |EC|)$$

$$= - \ln \left( \frac{|EC - q|}{EC} \right)$$

$$- \frac{t}{RC} = \ln \left( \frac{|EC - q|}{EC} \right)$$

$$e^{-\frac{t}{RC}} = \frac{EC - q}{EC}$$

$$EC e^{-t/RC} = EC - q$$

$$EC e^{-t/RC} - EC = -q$$

$$q = EC (1 - e^{-t/RC})$$

↑  
q<sub>max</sub>

- RC is time constant
- it determines how long charging / discharging occurs.
- In parallel, the time needed for discharge is longer than in series.

## Celebration #2 (chapter 7 - 10)

- No Gauss, No Magnetism
- $\vec{E}$  (Electric field lines, equipotential lines, ...)
- $\vec{E}$  (vectors  $\Rightarrow$  superposition) As opposed to scalars




- $W_{\text{Ext}} = \Delta E_{\text{PE}} = q_i \Delta V$

- Conservation of Energy


-	+
$K_i + U_i = K_f + U_f$	

- Capacitors

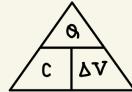

$$C = \frac{\kappa \epsilon_0 A}{d}$$


κ dielectric

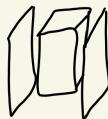

→ capacitance depends on the geometry &  $\kappa$

→  $\frac{\Delta V}{\Delta x} = E$  (in x-dir)
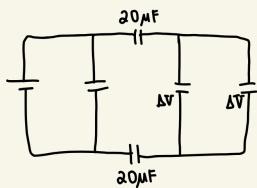
$$\frac{-\partial V}{\partial r} = \vec{E} \quad \text{so, } \left\langle -\frac{\partial V}{\partial x}, -\frac{\partial V}{\partial y}, -\frac{\partial V}{\partial z} \right\rangle \text{ N/C}$$



→ capacitors in series :  $Q$  (charges) same

→ " parallel :  $V$  (voltage) same


- RC Circuits

→ charging or discharging scenario ! Look @ the Question

charging  $\Rightarrow Q = Q_{\max} (1 - e^{-t/RC})$

discharging  $\Rightarrow Q = Q_{\max} e^{-t/RC}$

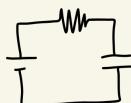} Remember, not going  
to be on paper/cheat sheet



- Pink worksheet on Resistors (10/19/2023)

→ Resistors | Bulbs


→ KIRCHHOFF'S RULE



$$I_{\text{bat}} = I_{6A} + I_{3A}$$

$$= 12A$$

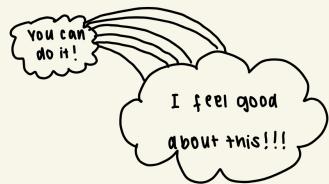if circuit is parallel,  
voltage is the same, so  
I is also the same  
for all ( $V = I \cdot R$ )




A circuit is constructed with 6 resistors and 2 batteries. The battery voltages are  $V_1 = 18V$  &  $V_2 = 12V$

$$R_1 = R_5 = 76\Omega \quad R_2 = R_6 = 137\Omega \quad R_3 = 66\Omega \quad R_4 = 101\Omega$$

$$I_1 + I_3 = 2I_{in}$$

$$I_2 = 2I_{in}$$

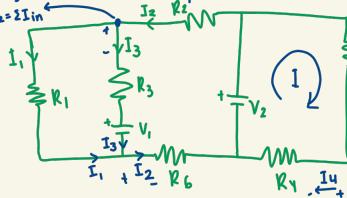

1) What is  $V_4$  the magnitude of the voltage across  $R_4$ ?

$$\text{loop 1 : } -I_4 R_5 - I_4 R_4 + V_2 = 0$$

$$-I_4 (R_5 + R_4) + V_2 = 0$$

$$I_4 = \frac{V_2}{R_5 + R_4} = \frac{12V}{76\Omega + 101\Omega} = \frac{12V}{177\Omega}$$

$$= 0.0678 A$$

$$V_4 = I_4 \cdot R_4$$

$$= (0.0678A)(101\Omega)$$

$$= 6.8478 V \approx 6.8 V_{//}$$

2) What is  $I_3$ , the current that flows through Resistor  $R_3$ ?

$$\text{Ans: } -0.122666 A$$

(A positive value for current is defined to be in the direction of the arrow)

3) What is  $I_2$  the current through  $R_2$ ? (A positive value is defined to be in direction of arrow)

$$\text{Ans: } 0.00766246 A$$

4) What is  $I_1$  current through  $R_1$ ? (+ value in direction of arrow)

$$\text{Ans: } 0.130316000 A$$